

CSE433

Proje 0

Bit Sequence Detector In Verilog

Lecturer: Alp Arslan Bayrakçı

Assistant: Fatma Nur Esirci

Table Of Contents

Table Of Contents	1
State Diagram	3
Truth Table	4
Karnaugh Maps For D-Flip Flops	5
Verifying Design With Behavioral Verilog	5
sqd_behavioral Module	5
sqd_behavioral Module Test Bench Results	6
Structural Verilog Implementation & Testbenches	7
d_flipflop Module Testbench	7
sqd_structural Module	8
sqd_structural Module Testbench	9
On Paper Design	11

State Diagram

Where:


A \rightarrow '-'

B \rightarrow '1'

C \rightarrow '10'

D \rightarrow '101'

E \rightarrow '1011'

 

Truth Table

Where:

State A → 3'b000

State B → 3'b001

State C → 3'b010

State D → 3'b011

State E → 3'b100

	Previous State				Input	Next State				Output
	Symbol	Q2	Q1	Q0	X	Symbol	Q2+	Q1+	Q0+	Z
0	A	0	0	0	0	A	0	0	0	0
1	A	0	0	0	1	B	0	0	1	0
2	B	0	0	1	0	C	0	1	0	0
3	B	0	0	1	1	B	0	0	1	0
4	C	0	1	0	0	A	0	0	0	0
5	C	0	1	0	1	D	0	1	1	0
6	D	0	1	1	0	C	0	1	0	0
7	D	0	1	1	1	E	1	0	0	0
8	E	1	0	0	0	C	0	1	0	0
9	E	1	0	0	1	A	0	0	0	1
10	-	1	0	1	0	-	X	X	X	X
11	-	1	0	1	1	-	X	X	X	X
12	-	1	1	0	0	-	X	X	X	X
13	-	1	1	0	1	-	X	X	X	X
14	-	1	1	1	0	-	X	X	X	X
15	-	1	1	1	1	-	X	X	X	X

There is no need to add D-Flip Flops to the truth table since they will be the same as the 'Next State'.

Karnaugh Maps For D-Flip Flops

Where:

$A \rightarrow Q2$

$B \rightarrow Q1$

$C \rightarrow Q0$

$D \rightarrow X$

$D2 : B.C.D \rightarrow \text{map}$

$= Q1.Q0.X$

$D1 : CD' + AD' + BC'D \rightarrow \text{map}$

$= Q0.X' + Q2.X' + Q1.Q0'.X$

$D0 : A'B'D + A'C'D \rightarrow \text{map}$

$= Q2'.Q1'.X + Q2'.Q0'.X$


Links are from an online tool to solve karnaugh maps called <http://www.32x8.com>.

Verifying Design With Behavioral Verilog

sqd_behavioral Module

```
1  /
2
3  8      reg [2:0] Q = 3'b000;
4
5  9
6
7  10     always @(posedge CLK, posedge RESET)
8
9  11     begin
10
11  12         $monitor("Q:%b, X:%b, Z:%b", Q,X,Z_OUT);
12
13  13         if(RESET == 1)
14
15  14             Q = 3'b000;
16
17  15
18  16     else begin
19
20  17         Q[2] <= (Q[1] & Q[0] & X);
21
22  18         Q[1] <= (Q[0] & ~X) | (Q[2] & ~X) | (Q[1] & ~Q[0] & X);
23
24  19         Q[0] <= (~Q[2] & ~Q[1] & X) | (~Q[2] & ~Q[0] & X);
25
26  20     end
27
28  21     end
29
30  22
31  23     assign Z_OUT = Q[2] & ~Q[1] & ~Q[0] & X;
32
33  24     endmodule
```

sqd_behavioral Module Test Bench Results

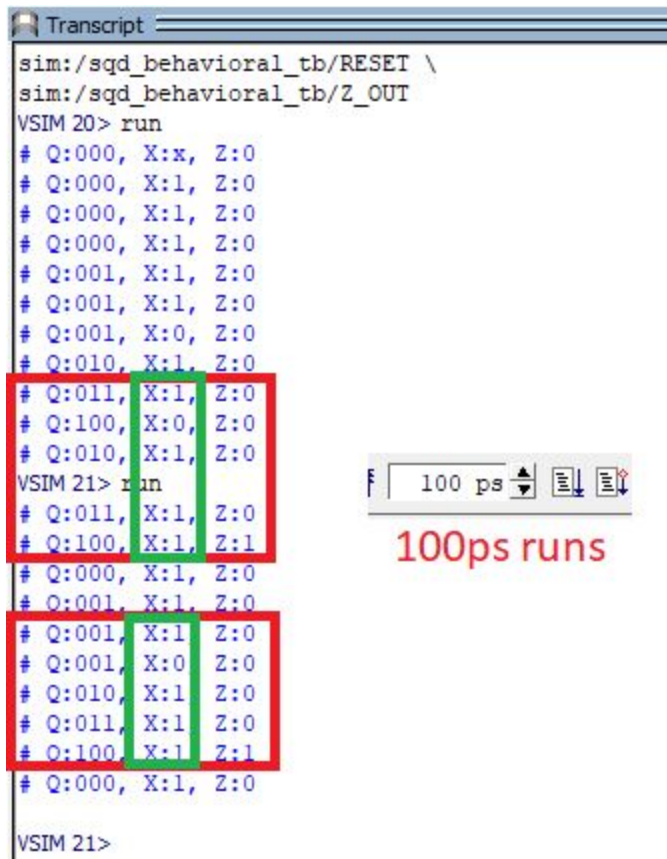

```
Transcript
sim:/sqd_behavioral_tb/RESET \
sim:/sqd_behavioral_tb/Z_OUT
VSIM 20> run
# Q:000, X:x, Z:0
# Q:000, X:1, Z:0
# Q:000, X:1, Z:0
# Q:000, X:1, Z:0
# Q:001, X:1, Z:0
# Q:001, X:1, Z:0
# Q:001, X:0, Z:0
# Q:010, X:1, Z:0
# Q:011, X:1, Z:0
# Q:100, X:0, Z:0
# Q:010, X:1, Z:0
VSIM 21> run
# Q:011, X:1, Z:0
# Q:100, X:1, Z:1
# Q:000, X:1, Z:0
# Q:001, X:1, Z:0
# Q:001, X:1, Z:0
# Q:001, X:0, Z:0
# Q:010, X:1, Z:0
# Q:011, X:1, Z:0
# Q:100, X:1, Z:1
# Q:000, X:1, Z:0
VSIM 21>
```

100 ps

100ps runs

Design is working correctly, the FSM flow is right. We continue with structural implementation next.

Structural Verilog Implementation & Testbenches

d_flipflop Module Testbench

```

 8  initial begin
 9
10      $monitor("D=%b, RESET=%b, CLK=%b, Q=%b, QN=%b",D,RESET,CLK,Q,QN);
11
12      CLK = 0;
13
14      D=0; RESET=0;
15
16      #2 D=1; RESET=0;
17      #2 D=1; RESET=1;
18      #2 D=0; RESET=0;
19
20  end
21  always #2 CLK=~CLK;
22 endmodule
```

```

VSIM 23> run
# D=0, RESET=0, CLK=0, Q=x, QN=x
# D=1, RESET=0, CLK=1, Q=1, QN=0
# D=1, RESET=1, CLK=0, Q=1, QN=0
# D=0, RESET=0, CLK=1, Q=0, QN=1
# D=0, RESET=0, CLK=0, Q=0, QN=1
# D=0, RESET=0, CLK=1, Q=0, QN=1
# D=0, RESET=0, CLK=0, Q=0, QN=1
# D=0, RESET=0, CLK=1, Q=0, QN=1
# D=0, RESET=0, CLK=0, Q=0, QN=1
# D=0, RESET=0, CLK=1, Q=0, QN=1
```

This module is working correctly.

sqd_structural Module

```
1  module sqd_structural(  
2      input CLK,  
3      input X,  
4      input RESET,  
5      output Z_OUT  
6  );  
7  
8      wire Q0,Q0N,Q1,Q1N,Q2,Q2N; //State Bits  
9      wire A1,A2,A3,A4,A5;      //Gate output wires  
10     wire D0,D1,D2;           //D Flip-Flop inputs  
11     wire XN;                  //Inverse of input bit X  
12  
13     //State Registers  
14     d_fflop ff0(D0,RESET,CLK,Q0,Q0N);  
15     d_fflop ff1(D1,RESET,CLK,Q1,Q1N);  
16     d_fflop ff2(D2,RESET,CLK,Q2,Q2N);  
17  
18     //Next State Logic  
19     not I1 (XN, X);  
20  
21     //D2 In  
22     and G1 (D2, Q1,Q0,X);  
23  
24     //D1 In  
25     and G2 (A1, Q0,XN);  
26     and G3 (A2, Q2,XN);  
27     and G4 (A3, Q1,Q0N,X);  
28     or  G5 (D1, A1,A2,A3);  
29  
30     //D0 In  
31     and G6 (A4, Q2N,Q1N,X);  
32     and G7 (A5, Q2N,Q0N,X);  
33     or  G8 (D0, A4,A5);  
34  
35     //Output Logic  
36     and G9 (Z_OUT, Q2,Q1N,Q0N,X);  
37  
38     always @(posedge CLK)  
39     begin  
40         $monitor("Q:%b%b%b, X:%b, Z:%b", Q2,Q1,Q0, X,Z_OUT);  
41     end  
42  
43     endmodule  
44
```


sqd_structural Module Testbench

```
1  module sqd_structural_tb;
2
3  reg CLK;
4  reg X;
5  reg RESET;
6  wire Z_OUT;
7
8  integer seed, i;
9
10 sqd_structural sqd(CLK, X, RESET, Z_OUT);
11
12 initial begin
13     CLK = 0;
14     forever #5 CLK = ~CLK;
15 end
16
17 initial begin
18     RESET = 1;
19     #30;
20     RESET = 0;
21 end
22
23 always @(posedge CLK)
24 begin
25
26     i = $urandom%20;
27     if(i > 2)
28         X = 1;
29     else
30         X = 0;
31
32     //$monitor("time = %4.1t, X = %b, Z_OUT = %b", $time, X, Z_OUT);
33 end
34
35
36
37
38 endmodule
39
```

This testbench generates random bits. Approximately %10 of bits are '0', %90 of bits are '1'.

```
sim:/sqd_structural_tb/CLK \  
sim:/sqd_structural_tb/X \  
sim:/sqd_structural_tb/RESET \  
sim:/sqd_structural_tb/Z_OUT
```

```
VSIM 26> run
```

```
# Q:000, X:1, z:0  
# Q:000, X:1, z:0  
# Q:000, X:1, z:0  
# Q:00x, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:0, z:0  
# Q:010, X:1, z:0
```

```
# Q:011, X:1, z:0  
# Q:100, X:0, z:0  
# Q:010, X:1, z:0
```

```
run
```

```
# Q:011, X:1, z:0  
# Q:100, X:1, z:1
```

```
# Q:000, X:1, z:0  
# Q:001, X:1, z:0
```

```
# Q:001, X:1, z:0  
# Q:001, X:0, z:0  
# Q:010, X:1, z:0  
# Q:011, X:1, z:0  
# Q:100, X:1, z:1
```

```
# Q:000, X:1, z:0
```

```
run
```

```
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0
```

```
run
```

```
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:1, z:0
```

```
VSIM 27> run
```

```
# Q:001, X:0, z:0
```

```
# Q:010, X:1, z:0  
# Q:011, X:0, z:0  
# Q:010, X:1, z:0  
# Q:011, X:1, z:0  
# Q:100, X:1, z:1
```

```
# Q:000, X:1, z:0  
# Q:001, X:1, z:0  
# Q:001, X:0, z:0  
# Q:010, X:0, z:0
```

```
VSIM 27>
```

On Paper Design

In case there is a typo in the tables or FSM in the report, here is the original design.

